

# **Group - 9**

## **Rechargeable Battery Charger with Indicator**

**Prepared under guidance of:**

- Prof. Ashok Ranade


**Prepared by:**

- Om Thakkar (201501109)
- Harshil Shah (201501097)
- Kirtan Gajjar (201501029)
- Shivam Agrawal(201501004)

**Semester: 1**


**School of Engineering and Applied Sciences,  
Ahmedabad University**

## BLOCK DIAGRAM:

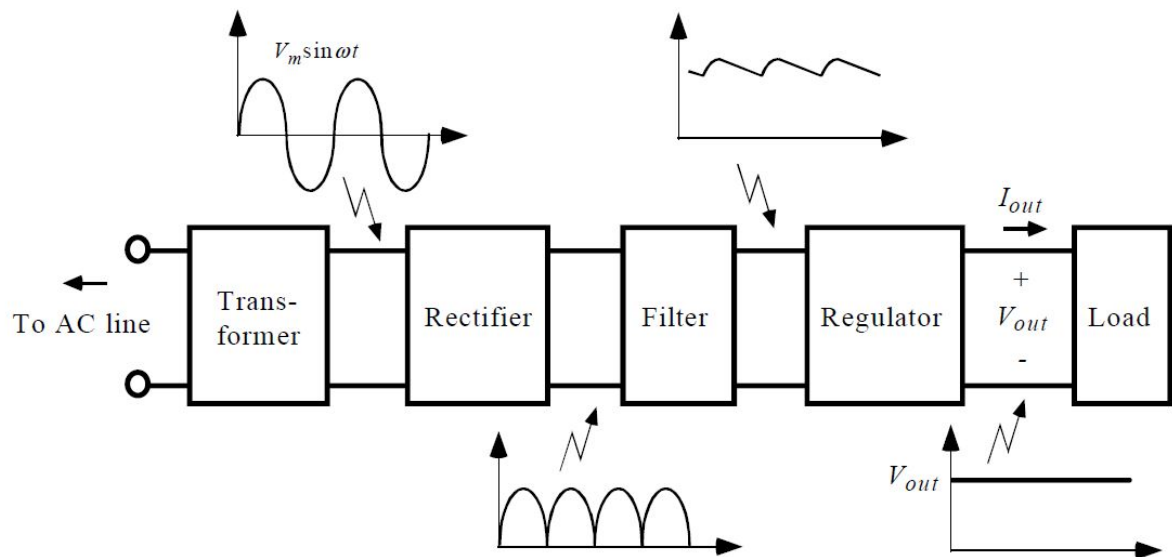

Components of a typical linear power supply

## CIRCUIT (Charging):

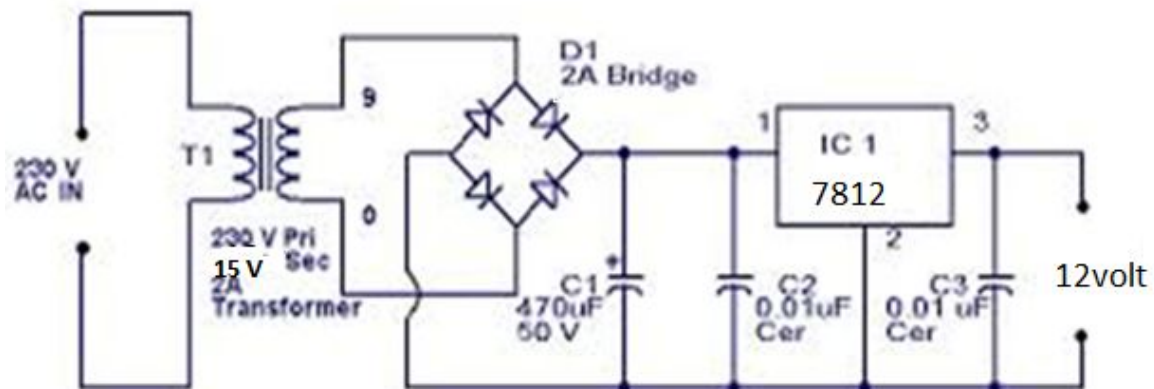

## **COMPONENTS:**

- Transformer (15V) – 1
- Rectifier Diodes – 1
- Capacitors:
  - 1) 470uF – 1
  - 2) 0.01uF – 2
- IC 7812 (Voltage Regulator)


## **Further Information**

- Input Voltage : 230V
- Step down Transformer : Transformed to 12V

## **Readings & Circuit Information:**

- The Circuit contains a 15V step- down transformer (A transformer is an electrical device that transfer energy between two or more circuit through electromagnetic induction) with 4 “1N4007” diodes as Rectifier Circuit to Rectify AC voltage into DC voltage.
- About IC7812:
  - 1<sup>st</sup> pin is connected in Parallel with 470uF and 0.01uF Resistor and with diode as shown in the circuit while 3<sup>rd</sup> pin is connected with 0.01uF Resistor and output. Here 2<sup>nd</sup> pin is connected with other terminal of 1<sup>st</sup> and 3<sup>rd</sup> pin's components.
  - This whole setup is expected to give output voltage of 12V DC Voltage.
  - Experimental Voltage : 12.18V
  - Error :  $(0.18/12)*100 = 1.5\%$ .

## CIRCUIT (Indicator):

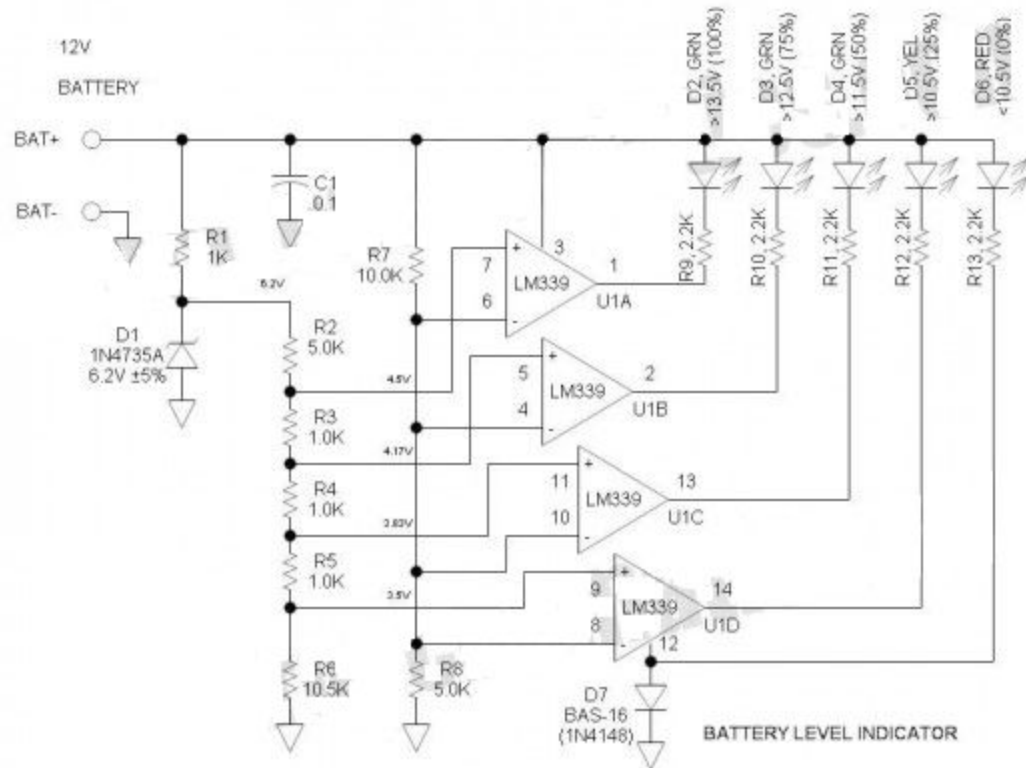

## **COMPONENTS:**

➤ **IC : LM339**

➤ **ZENER diode:**

1) 1N4735A - 1

2) 1N4148 - 1

➤ **RESISTORS:**

1) 2.2k $\Omega$  - 4

2) 1k $\Omega$  - 4

3) 10.5k $\Omega$  - 1

4) 5.0k $\Omega$  - 2

5) 10k $\Omega$  - 1

➤ **CAPACITOR:**

1) 0.1 $\mu$ F - 1

➤ **LEDs:**

1) Green - 3

2) Yellow - 1

3) Red - 1

## **Further Information**

➤ **Input Voltage : 12V**

## **Readings & Circuit Information:**

- Here we have made a circuit having an IC equivalent to 4 operational amplifiers namely LM339 with different resistors in order to get indication of LEDs at certain specific amount of voltages.
- Experimented Result obtained are as follows:

Indication	Voltage
LED1 (0%)	1.8
LED2 (25%)	10.8
LED3 (50%)	11.8
LED4(75%)	12.9
LED5 (100%)	13.9

- Thank You